

# EE362 Induction Machine

Nail Tosun - 2094563

Electric and Electronic Engineering Department, METU

2018

April

## Induction Motor Tests

### No-load test

It is the same as open circuit test of transformer. It gives information about *rotational loss* and *excitation current*.

Since there is no load;

$$s = 0$$

Then equivalent circuit becomes;

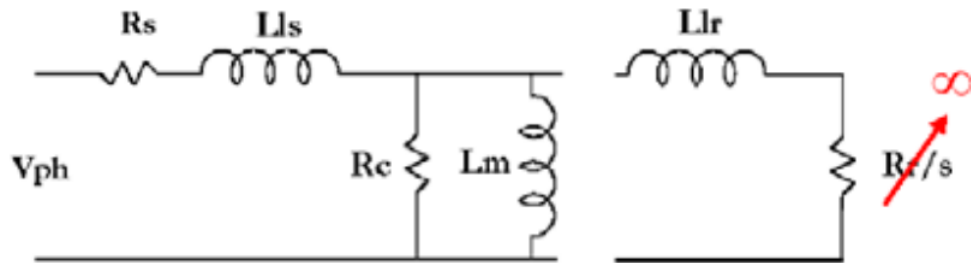


Figure 1: No-load equivalent circuit

The values we obtain from no load test are;

Table 1: test result				
$V_{line}$	$I_0$	$I_{max}$	P	$f_s$
208 V	1.5A	1.7 A	49	60 Hz

$$V_{ph} = \frac{208}{\sqrt{3}} = 121.1V$$

$$\cos(\phi) = \frac{\frac{P_{3\phi}}{3}}{V_{ph}I_{Ph}} = 0.09$$

$$\phi = 84.8 \text{ deg}$$

$$I_m = I_0 \sin(\phi) = 1.485A$$

$$I_c = I_0 \cos(\phi) = 0.135A$$

Now assuming  $R_c$  is much greater than  $R_s$ ;

$$L_m = X_m = \frac{V_{ph}}{2\pi f_s I_m}$$

$$L_m = 0.23H$$

$$R_c = \frac{V_{ph}}{I_c}$$

$$R_c = 900\text{ohm}$$

### Locked rotor test

Since rotor is stationary with mechanical brake,  $f_r = 0$  and

$$s = 1$$

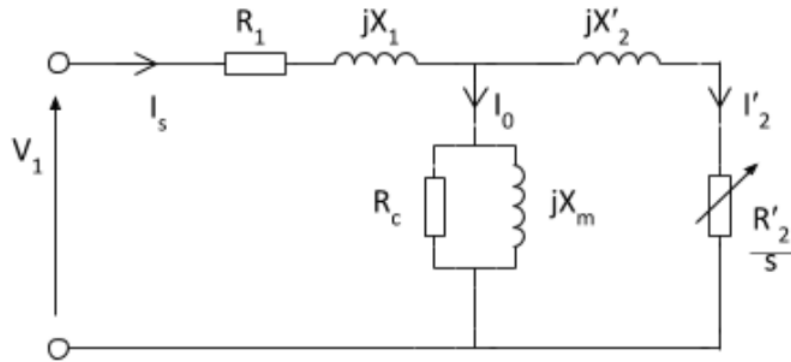


Figure 2: Locked-rotor test equivalent circuit

Find  $R_1$  with dc resistance test. How?

### DC resistance test

If machine is Y-connected, put dc supply (low voltage reference to its rated) measure the current.

$$2R_Y = \frac{V_{in}}{I_{measured}}$$

$$R_Y = \frac{1}{2} \frac{V_{in}}{I_{measured}}$$

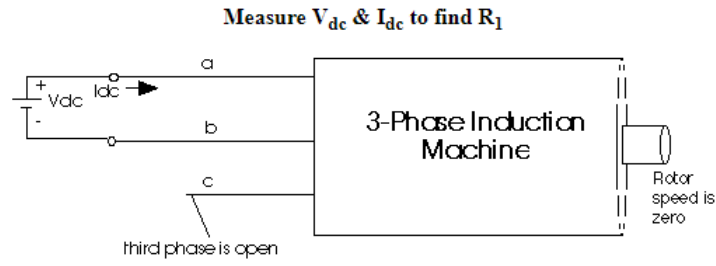


Figure 3: Testing dc resistance for Y-connected ac machine

If ac machine delta connected,

$$\frac{V_{in}}{I_{measured}} = R_d || 2R_d$$

$$R_d = \frac{3}{2} \frac{V_{in}}{I_{measured}}$$

Now ac resistance of  $R_1$  is approximately  $R_{1_{ac}} = 1.1R_{1_{dc}}$

$$V_{ph} = I$$

### Example

For an induction motor following test results are obtained;

	Table 2: Test results		
	Line voltage	Line current	Input power
Locked rotor test	130 V	77 A	6.4 kW
No-load test	415 V	22.8 V	1.65 kW

Machine rating; 30kW 3-ph, 50 Hz, 4-pole, 415 V, delta-connected

$$r_{1dc} = 0.44 \text{ ohm}$$

Assume  $X_1 = X_2$

**Solution**

$$r_{1ac} = 1.1r_{1dc} = 0.48 \text{ ohm}$$