

# EE314 Experiment 5 Flip-Flops and Sequential Circuits

Nail Tosun - 2094563  
Electric and Electronic Engineering Department, METU

2018  
April

1)

 


Figure 1: Logic design for Question 1

2)

$$\begin{aligned}
 Q_{1n} &= JQ'_{1n-1} + K'Q_{1n-1} \\
 J &= Q'_{3n-1}Q'_{2n-1} \quad K = Q_{3n-1}Q_{2n-1} \\
 K' &= Q'_{3n-1} + Q'_{2n-1} \\
 Q_{1n} &= Q'_{3n-1}Q'_{2n-1}Q'_{1n-1} + (Q'_{3n-1} + Q'_{2n-1})Q_{1n-1} \\
 Q_{2n} &= JQ'_{2n-1} + K'Q_{2n-1} \\
 J &= Q_{1n} \quad K' = Q_{1n} \\
 Q_{2n} &= Q_{1n}Q'_{2n-1} + Q_{1n}Q_{2n-1} \\
 Q_{2n} &= 2Q_{3n-1}Q'_{2n-1}Q'_{1n-1} + Q'_{2n-1}Q_{1n-1} + Q_{2n-1}Q_{1n-1}Q'_{3n-1} \\
 Q_{3n} &= JQ_{3n-1} + KQ'_{3n-1} \\
 J &= Q_{2n} \quad K = Q_{2n} \\
 Q_{3n} &= 2Q_{3n-1}Q'_{2n-1}Q'_{1n-1} + Q_{3n-1}Q'_{2n-1}Q_{1n-1}
 \end{aligned}$$

3)

 


Figure 2: Frequency Converter Logic Design

4)

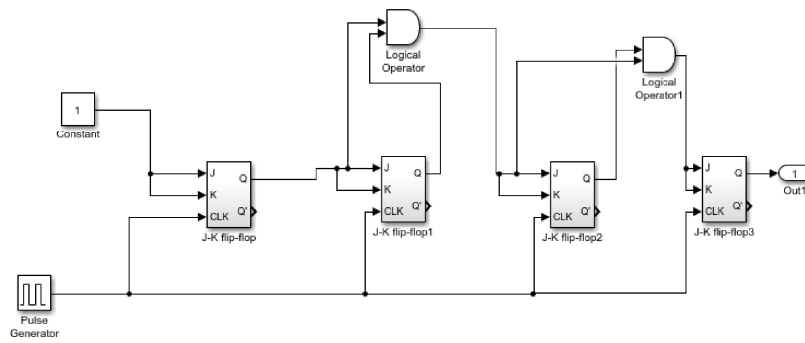


Figure 3: Ripple Up Counter

5)

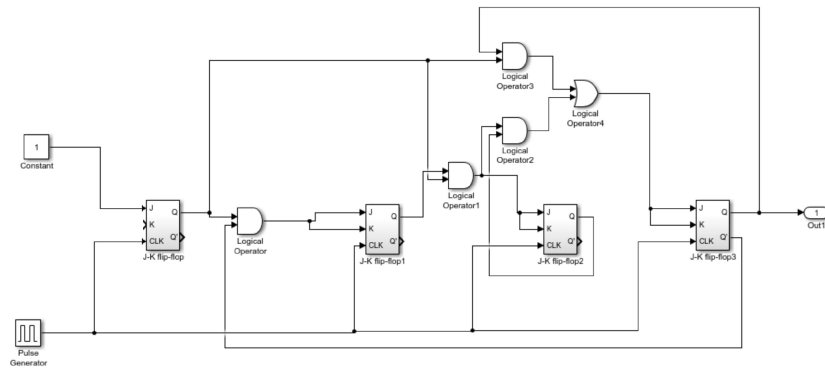


Figure 4: BCD counter

6)

```

module counter(clr,clk,dir, tc, q);
    input clr,clk,dir;
    output reg tc;
    output reg[3:0] q;
    always@(posedge clk,posedge clr)
    begin
        if(clr==1)
            q=4'd0;
        else
            begin
                if (dir==1)
                    q=q+1;
                else if(dir==0)
                    q=q-1;
                if(dir==1 & q==4'd10)
                    begin
                        q=4'd0;tc=1'b1;
                    end
                else if(dir==0 & q==4'd15)
                    begin
                        q=1'd9;tc=1'b1;
                    end
                else tc=1'b0;
            end
    end
endmodule

```

Figure 5: Verilog Code

 


Figure 6: BCD counter Simulation results