

# EE312 Take-Home Exam 2

Nail Tosun - 2094563  
Electric and Electronic Engineering Department, METU

2018  
March

- 1) The reason of  $R_{B_2}$  is when output switch high to low it creates a discharge path for internal capacitances of second transistor. When  $V_{IN} < 2.8$  since  $Q_2$  transistor will be off and output voltage equal  $V_{cc}$ . With increasing  $V_{in}$  pushes  $Q_2$  to saturation region therefore  $V_{out} = 0.2V$

$$V_{IL} = 2.8V, V_{IH} = 2.9V, V_{OL} = 0.2V, V_{OH} = 6V$$

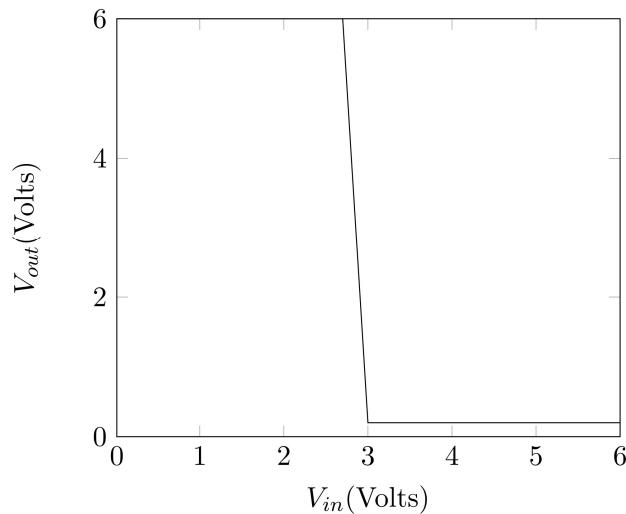


Figure 1: Voltage Transfer Characteristic

Region 1:  $0 < V_{IN} < 2.8$    Region 2:  $2.8 < V_{IN} < 2.9$    Region 3:  $2.9 < V_{IN} < 6$

Table 1: Operation Regions of Transistors and Diodes

	Region 1	Region 2	Region 3
Q1	Cut-Off	Forward Active	Forward Active
Q2	Cut-Off	Forward Active	Saturation
D1	On	On	On/Off
D2	Off	On	On
D3	Off	On	On
D4	Off	On	On

$$NMH = V_{OH} - V_{IH} = 3.1V$$

$$NML = V_{IL} - V_{OL} = 2.6V$$

For fan-out calculations there are two cases;

Output HIGH case: Since there is  $D_1$  diode connected there is no current come from load to driver gate. Therefore we can connect infinitely many load gate.

$$N_H = \infty$$

Output LOW case:

$$I_{C_2} = \frac{V_{cc} - V_{sat}}{12k} + \frac{V_{cc} - V_{D_1} - V_{sat}}{4.7k}$$

$$I_{C_2} = 16.76mA$$

$$\max(I_{C_2}) = \beta_F \sigma I_{B_1}$$

$$I_{B_1} = \frac{V_{cc} - V_{B_1}}{(1 - \rho)R_{B_1} + \rho R_{B_1}\beta_F}$$

$$I_{B_2} = \frac{0.8}{60k} + 36 \frac{6 - 3.6}{((1 - \rho) + 36\rho)4.7k}$$

$$16.76mA = \sigma(0.013 + \frac{18.38}{((1 + 35\rho)4.7k)})\beta_F$$

$$35\rho + 1 = 31.39$$

$$\rho = 0.85$$

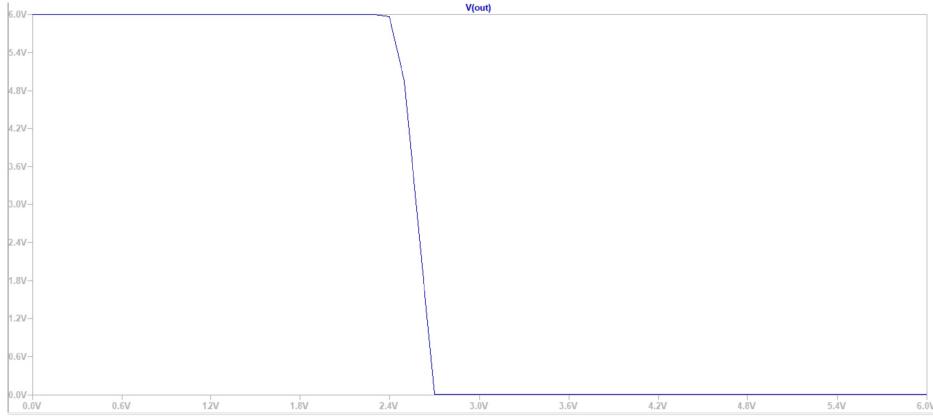


Figure 2: LTspice simulation results

2)

Table 2: Operation Regions of Transistors and Diodes

	Region 1	Region 2	Region 3	Region 4
Q1	Saturation	Saturation	Saturation	Reverse-Active
Q2	Cut-Off	Forward Active	Saturation	Saturation
Q3	Forward Active	Forward Active	Saturation-FA	Cut-Off
Q4	Cut-Off	Cut-Off	Forward-Active	Saturation
D1	On	On	On	Off
D2	On	On	On	On

Region 1 :  $0V \leq V_{in} \leq 0.5V$   $Q_1$  is in saturation region since collector is connected to  $Q_2$ 's base. Since  $V_{CEQ_1} = 0.2V + V_{in}$  in this region  $Q_2$  is in cut-off region. If  $Q_2$  is cut-off region its emitter and collector current is zero. Therefore  $Q_4$ 's base is ground therefore  $Q_4$  is also cut-off region.  $D_1$  diode and  $D_2$  diode is open since they are positively bias. For  $Q_3$

$$V_B = 4.3V, V_C = 5V, V_E = 3.6V$$

Therefore it is forward active region.

$$V_{out} = 3.9V$$

Region 2:  $0.5 \leq V_{in} < 1.2V$  in this region  $Q_2$  is open but since there is enough potential at  $Q_4$  base still  $Q_4$  is in cut-off region.  $V_{out}$  decreases with

linearly since t since it collector's( $Q_2$ ) voltage fall :

$$V_{out} = V_C - V_{D_1} - V_{D_2} - 0.7$$

$Q_1$  is saturation region. Diodes are open but since  $Q_4$  off there is still no current(floating output).  $Q_1$  is still saturated. At that point:

$$V_{out} = 6 - \beta_F I_B - V_{D_1} - V_{D_2} - 0.7$$

Region 3:  $1.2V \leq V_{in} \leq V_x$  When input hit 1.2V now  $Q_4$  will open.  $Q_1$  still in saturation.  $V_{out}$  drops very quick since  $Q_2$  collector voltage drop will faster due to  $Q_4$  opening.

Region 4: When  $Q_2$  collector voltage drop 2.1 V since  $Q_3$  will be off (not enough voltage at BE junction) no current will appear at output. This forces  $Q_4$  to saturation and  $V_{out}$  is fitted to 0.2 V which is output low voltage.

$V_{OL} = 0.2V$ ,  $V_{OH} = 3.9V$ ,  $V_{IL} = 0.5V$ ,  $V_{IH} = 1.4V$  Voltage Transfer Characteristic is following;

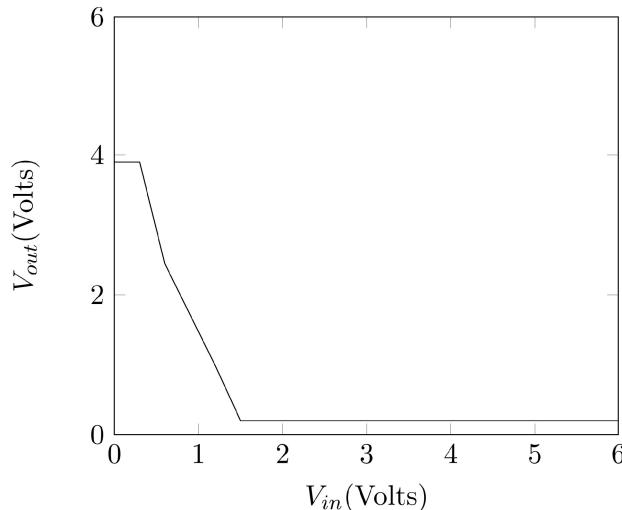


Figure 3: Voltage Transfer Characteristic

For Fan-out calculation:

1)Output high case

$$V_{out} = V_{IH} + NMH, VIH = 1.4V NMH = 1V$$

$$V_{out} = 2.4V$$

Assuming  $Q_3$  is in forward active region. Therefore  $I_{C3} = \beta_F I_{B3}$

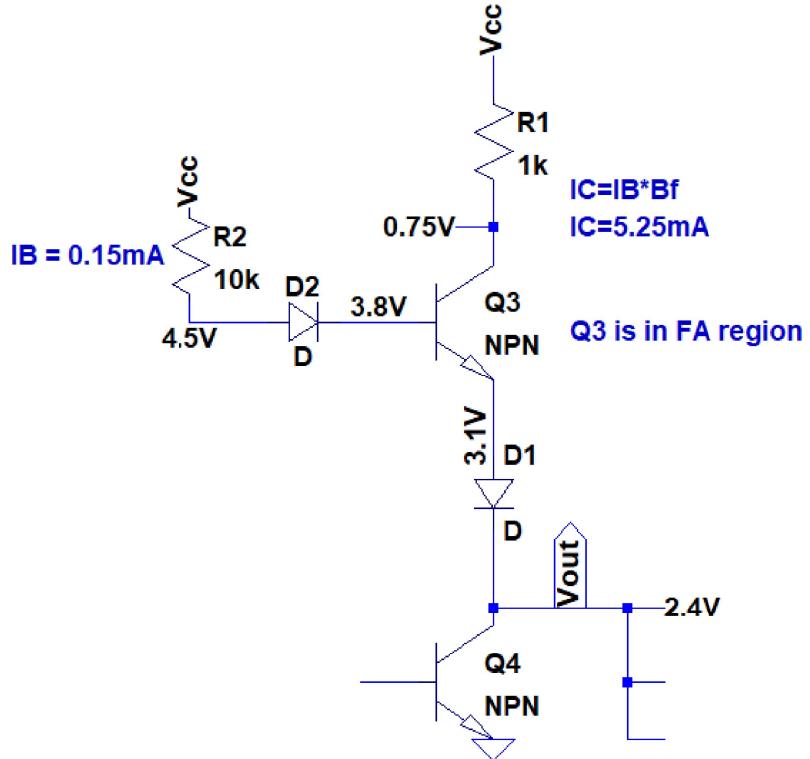


Figure 4: Assuming  $Q_3$  in FA region

Since  $V_{C3} = 0.75$  it is not in FA region. Next assuming is it is in saturation region.

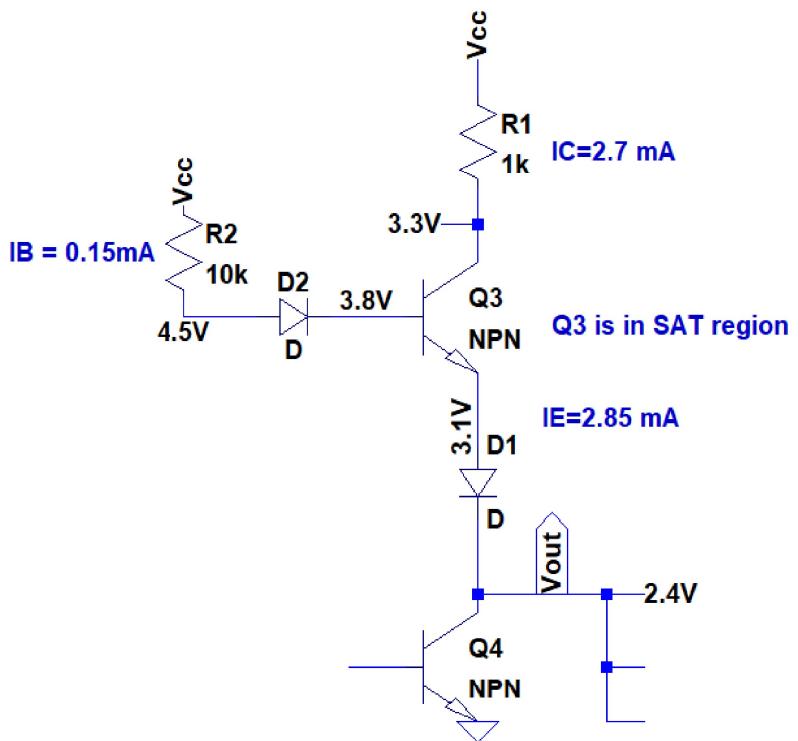


Figure 5: Assuming  $Q_3$  in SAT region

Now all the voltage values make sense.  $I_{OH} = 2.85\text{mA}$

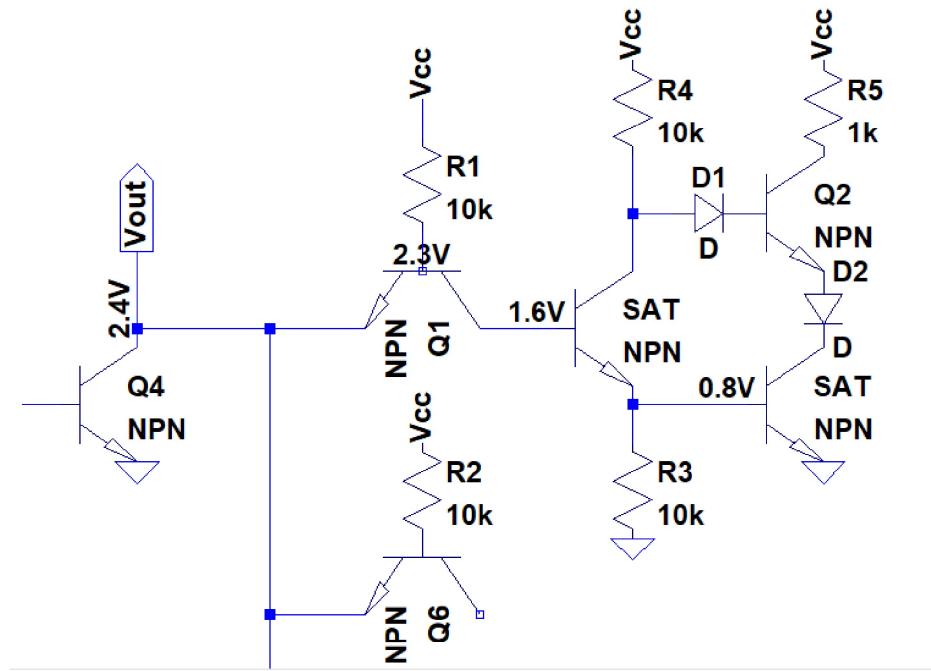


Figure 6: Maximum fan-out calculation

$$I_{B1} = 0.37mA \quad I_{E1} = \beta_R I_{B1} = 0.74mA$$

$$\frac{I_{OH}}{I_{E1}} = 3.85$$

$$N = 3$$

Output low case; Driver gate is following:

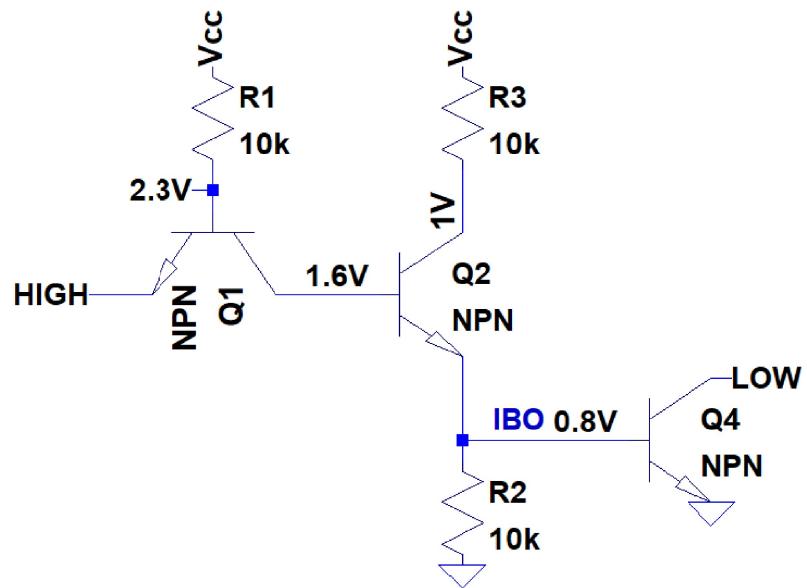


Figure 7: Driver gate

$$I_{B_1} = 0.37mA, \quad I_{C_1} = (\beta_R + 1)I_{B_1} \quad I_{C_2} = 0.5mA$$

$$I_{BO} = (0.5 + 1.11 - 0.08)mA = 1.53mA$$

$$\sigma_o = \frac{I_{C_{max}}}{\beta_F I_{BO}}$$

$$I_{C_{max}} = 42.84mA$$

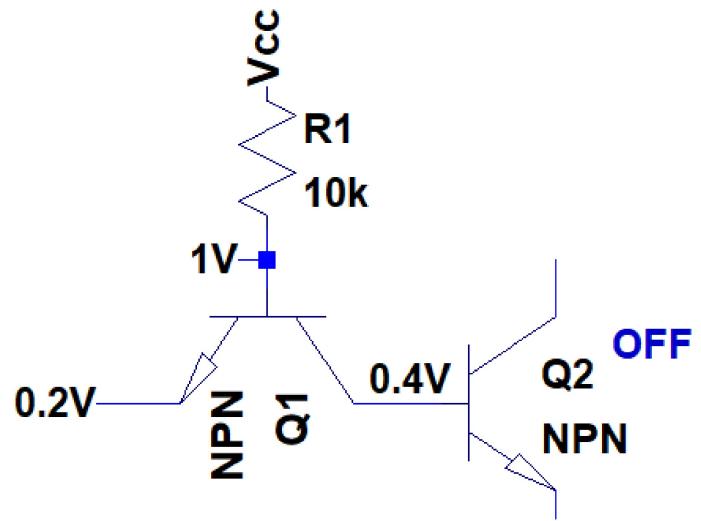


Figure 8: Load gate

$$N = \frac{42.84}{0.5} = 85$$

Maximum fan-out: 3=min(85,3)

Power Consumption: Output low case:  $P_L = 6(0.15) + 6(0.5) = 3.90mW$   
 Output high case:  $= 6(0.5) = 3mW$   $P_{average} = 3.45mW$